

[A]

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \quad \text{Open ckt. dr. pt. i/p ad.}$$


$$* g_{11} = \frac{1}{V_1/I_1} \Big|_{I_2=0} \Rightarrow g_{11} = \frac{1}{z_{11}}$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0} \quad \text{Open ckt. for. vol. gain}$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0} \quad \text{Short Ckt. rev. cur. gain}$$

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} \quad \text{Short ckt. dr. pt. o/p imp.}$$

$$* g_{22} = \frac{1}{I_2/V_2} \Big|_{V_1=0} \Rightarrow g_{22} = 1/Y_{22}$$

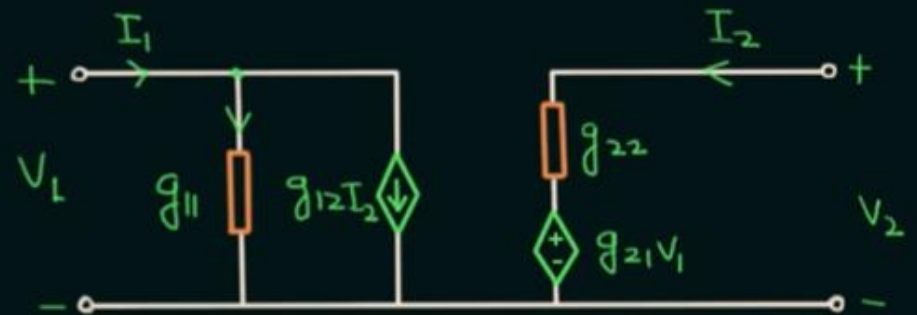

$h \rightarrow g :-$

$$g_{11} = h_{22}/|h_{11}| \quad g_{12} = -h_{12}/|h_{11}|$$

$$g_{21} = -h_{21}/|h_{11}| \quad g_{22} = h_{11}/|h_{11}|$$

$g \rightarrow h :-$

$$h_{11} = g_{22}/|g_{11}| \quad h_{12} = -g_{12}/|g_{11}|$$

$$h_{21} = -g_{21}/|g_{11}| \quad h_{22} = g_{11}/|g_{11}|$$

## ✓ Z-Parameters to g-Parameters Conversion

$$\check{V}_1 = Z_{11}\check{I}_1 + Z_{12}\check{I}_2 \text{ --- (i)}$$

$$\check{V}_2 = Z_{21}\check{I}_1 + Z_{22}\check{I}_2 \text{ --- (ii)}$$

$$\check{I}_1 = g_{11}\check{V}_1 + g_{12}\check{I}_2 \text{ --- (iii)}$$

$$\check{V}_2 = g_{21}\check{V}_1 + g_{22}\check{I}_2 \text{ --- (iv)}$$

$$V_1 - Z_{12}I_2 = Z_{11}I_1$$

$$\Rightarrow I_1 = \frac{1}{Z_{11}}V_1 - \frac{Z_{12}}{Z_{11}}I_2 \text{ --- (v)}$$

$$I_1 \rightarrow \text{(ii)} :-$$

$$V_2 = Z_{21}\left[\frac{1}{Z_{11}}V_1 - \frac{Z_{12}}{Z_{11}}I_2\right] + Z_{22}I_2$$

$$V_2 = \frac{Z_{21}}{Z_{11}}V_1 - \frac{Z_{21}Z_{12}}{Z_{11}}I_2 + Z_{22}I_2$$

$$V_2 = \frac{Z_{21}}{Z_{11}}V_1 + \left[Z_{22} - \frac{Z_{21}Z_{12}}{Z_{11}}\right]I_2$$

$$\frac{Z_{11}Z_{22} - Z_{21}Z_{12}}{Z_{11}} = \frac{|Z|}{Z_{11}}$$

$$V_2 = \frac{Z_{21}}{Z_{11}}V_1 + \frac{|Z|}{Z_{11}}I_2 \text{ --- (vi)}$$

$$g_{11} = \frac{1}{Z_{11}}$$

$$g_{12} = -\frac{Z_{12}}{Z_{11}}$$

$$g_{21} = \frac{Z_{21}}{Z_{11}}$$

$$g_{22} = \frac{|Z|}{Z_{11}}$$

$$g \rightarrow z :-$$

$$Z_{11} = 1/g_{11}$$

$$Z_{12} = -g_{12}/g_{11}$$

$$Z_{21} = g_{21}/g_{11}$$

$$Z_{22} = |g|/g_{11}$$



## ✓ ABCD-Parameters (or) Transmission Parameters

>> Also known as T-Parameters, Cascade Parameters and Chain Parameters.

$$V_s = \check{V}_1, I_s = \check{I}_1, V_r = \check{V}_2, I_r = -\check{I}_2$$

$V_r$  and  $I_r \rightarrow \text{ind.}$

$V_s$  and  $I_s \rightarrow \text{dep.}$

$$\begin{pmatrix} V_s \\ I_s \end{pmatrix} = f \begin{pmatrix} V_r \\ I_r \end{pmatrix}$$

$$V_s = AV_r + BI_r$$

$$I_s = CV_r + DI_r$$

$$V_1 = AV_2 + B(-I_2) \text{ — (i)}$$

$$I_1 = CV_2 + D(-I_2) \text{ — (ii)}$$

$$V_1 = AV_2 - BI_2 \text{ — (iii)}$$

$$I_1 = CV_2 - DI_2 \text{ — (iv)}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

↑  
[T]

t - parameters

(or)

I.T.P.

(or)

abcd par.



$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \text{Open ckt. rev. vol. gain}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \text{Open ckt. rev. tr. ad.}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \text{Short ckt rev. tr. imp.}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \quad \text{Short ckt rev. current gain}$$

## ✓ ABCD-Parameters to Z-Parameters Conversion

$$V_1 = AV_2 - BI_2 \quad \text{--- (i)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (ii)}$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (iii)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (iv)}$$

$$I_1 + DI_2 = CV_2$$

$$\Rightarrow V_2 = \frac{1}{C}I_1 + \frac{D}{C}I_2 \quad \text{--- (v)}$$

$$V_2 \rightarrow \text{(i)} :-$$

$$V_1 = A\left[\frac{1}{C}I_1 + \frac{D}{C}I_2\right] - BI_2$$

$$V_1 = \frac{A}{C}I_1 + \frac{AD}{C}I_2 - \underline{BI_2}$$

$$V_1 = \frac{A}{C}I_1 + \left[\frac{AD}{C} - B\right]I_2$$

$$\frac{AD}{C} - B = \frac{AD - BC}{C} = \frac{|T|}{C}$$

$$V_1 = \frac{A}{C}I_1 + \frac{|T|}{C}I_2 \quad \text{--- (vi)}$$

$$Z_{11} = \frac{A}{C}$$

$$Z_{12} = \frac{|T|}{C}$$

$$Z_{21} = \frac{1}{C}$$

$$Z_{22} = \frac{D}{C}$$

Z  $\rightarrow$  ABCD :-

$$A = \frac{Z_{11}}{Z_{21}}$$

$$B = \frac{|Z|}{Z_{21}}$$

$$C = \frac{1}{Z_{21}}$$

$$D = \frac{Z_{22}}{Z_{21}}$$




## Open Circuit & Short Circuit Impedances (in terms of ABCD-Parameters)


$$V_1 = AV_2 - BI_2 \quad \text{--- ①}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- ②}$$


1) Open Circuit i/p Impedance:

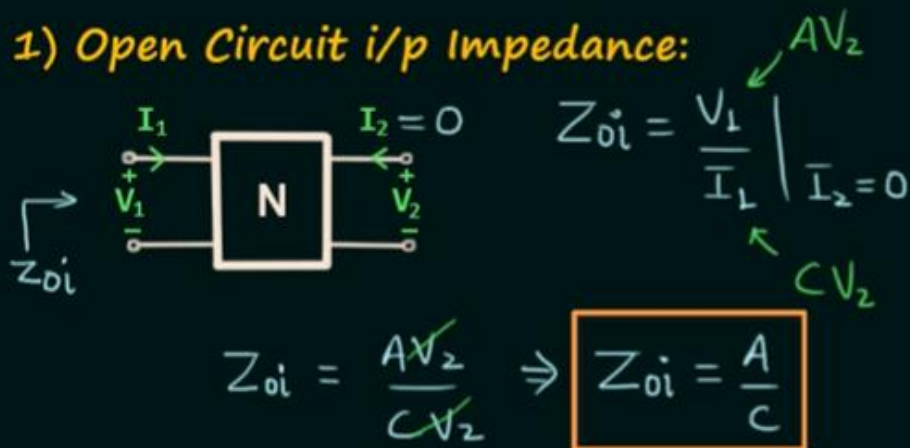

2) Open Circuit o/p Impedance:

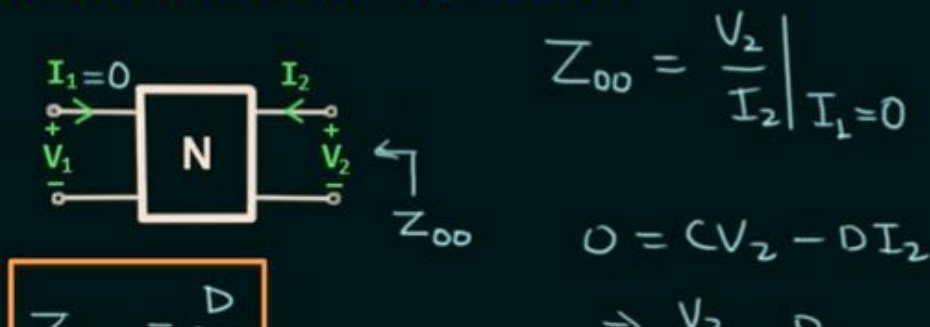


3) Short Circuit i/p Impedance:

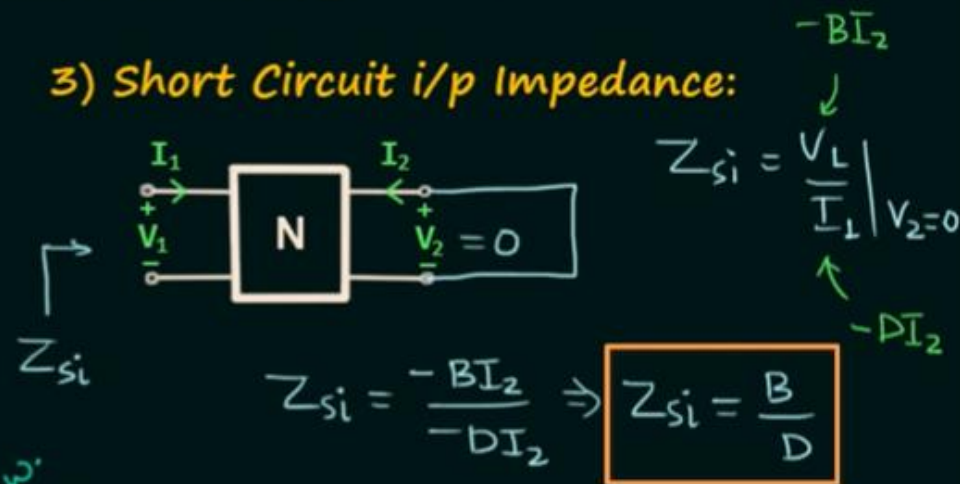


h.w.

4) Short Circuit o/p Impedance:

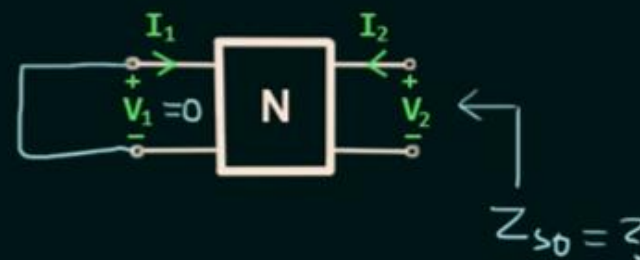

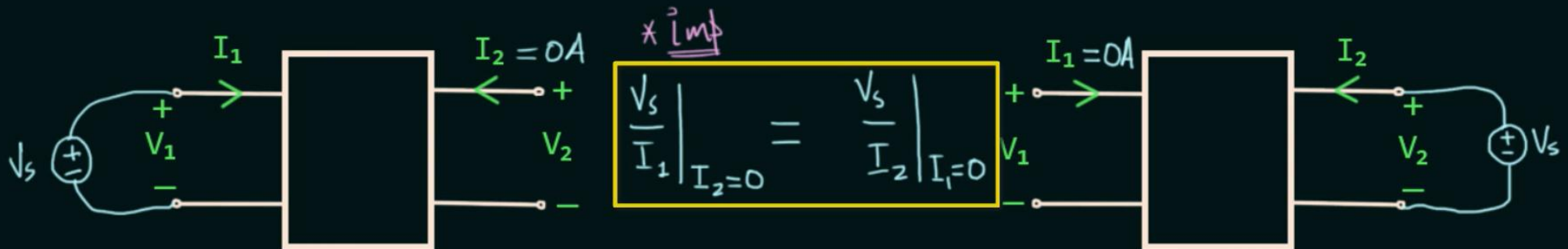
## Concept of Symmetry in Two-Port Networks

>> A two-port network is said to be symmetrical if the ratio of excitation to response remains the same at both the ports <sup>① and ②</sup> independently w.r.t. the defined circuit conditions such as open circuit or short circuit.



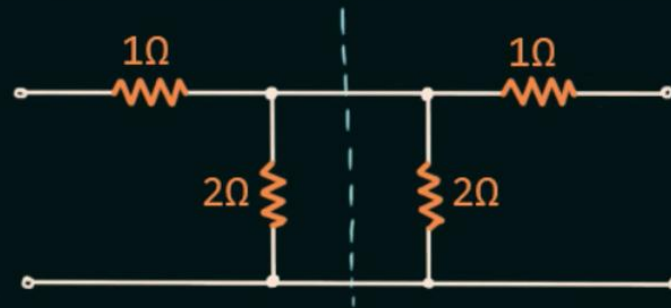**Note:** For small independent networks we can identify the symmetry using the mirror image property.



## Condition for Symmetry in Two-Port Networks

>> Condition for Symmetry:

$$\left. \frac{V_s}{I_1} \right|_{I_2=0} = \left. \frac{V_s}{I_2} \right|_{I_1=0}$$

>> In terms of Z-Parameters:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (i)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (ii)}$$

$$V_1 = V_s \text{ and } I_2 = 0$$

$$V_s = Z_{11}I_1 \Rightarrow \left. \frac{V_s}{I_1} \right|_{I_2=0} = Z_{11}$$

$$V_2 = V_s \text{ and } I_1 = 0$$

$$V_s = Z_{22}I_2 \Rightarrow \left. \frac{V_s}{I_2} \right|_{I_1=0} = Z_{22}$$

$$Z_{11} = Z_{22}$$

>> In terms of Y-Parameters:

$$\begin{aligned} Z_{11} &= Y_{22}/|Y| & Z_{22} &= Y_{11}/|Y| \\ \Rightarrow \frac{Y_{22}}{|Y|} &= \frac{Y_{11}}{|Y|} & \Rightarrow Y_{11} &= Y_{22} \end{aligned}$$

>> In terms of h-Parameters:

$$\begin{aligned} Z_{11} &= \frac{|h|}{h_{22}} & \Rightarrow \frac{|h|}{h_{22}} &= \frac{1}{h_{22}} & \Rightarrow |h| &= 1 \\ Z_{22} &= 1/h_{11} \end{aligned}$$

>> In terms of g-Parameters:


$$\begin{aligned} Z_{11} &= 1/g_{11} & \Rightarrow \frac{1}{g_{11}} &= \frac{|g|}{g_{11}} & \Rightarrow |g| &= 1 \\ Z_{22} &= |g|/g_{11} \end{aligned}$$

>> In terms of ABCD-Parameters:

$$Z_{11} = A/c \quad Z_{22} = D/c \Rightarrow \frac{A}{c} = \frac{D}{c} \Rightarrow A = D$$



## ✓ Series-Series Interconnection

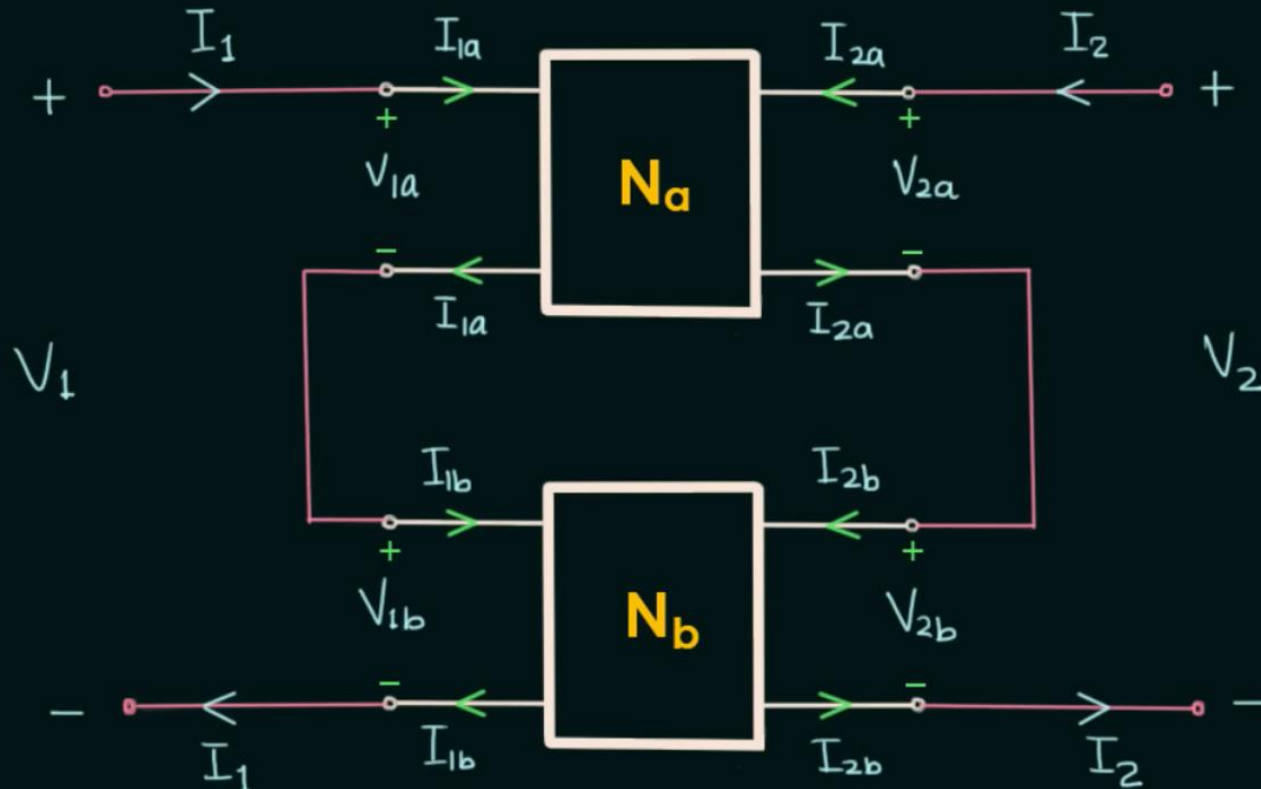

$$I_1 = I_{1a} = I_{1b}$$

$$I_2 = I_{2a} = I_{2b}$$

$$+V_1 - V_{1a} - V_{1b} = 0$$

$$V_1 = V_{1a} + V_{1b} \quad \text{--- ①}$$

$$V_2 = V_{2a} + V_{2b} \quad \text{--- ②}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [Z_a] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + [Z_b] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \underbrace{\{ [Z_a] + [Z_b] \}}_{[Z]} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

o imp.


$$[Z] = [Z_a] + [Z_b]$$

$$\rightarrow Z_{11} = Z_{11a} + Z_{11b}$$

$$[Z] = [Z_a] + [Z_b] + \dots + [Z_n]$$



## Parallel-Parallel Interconnection

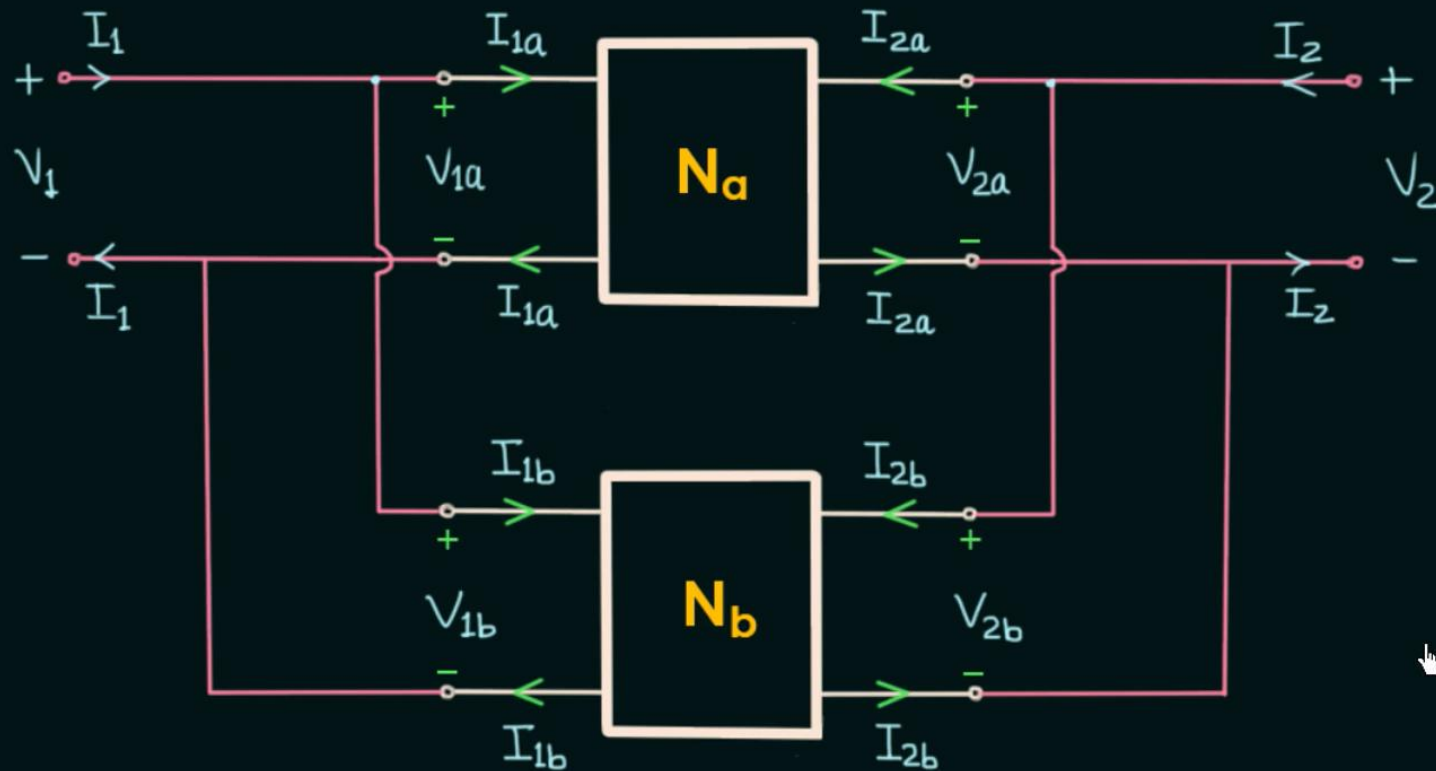

$$V_1 = V_{1a} = V_{1b}$$

$$I_1 = I_{1a} + I_{1b} \text{ --- (i)}$$

$$V_2 = V_{2a} = V_{2b}$$

$$I_2 = I_{2a} + I_{2b} \text{ --- (ii)}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} + \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [Y_a] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + [Y_b] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\{ [Y_a] + [Y_b] \}}_{[Y]} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[Y] = [Y_a] + [Y_b]$$

$$[Y] = [Y_a] + [Y_b] + \dots + [Y_n]$$

## ✓ Series-Parallel Interconnection

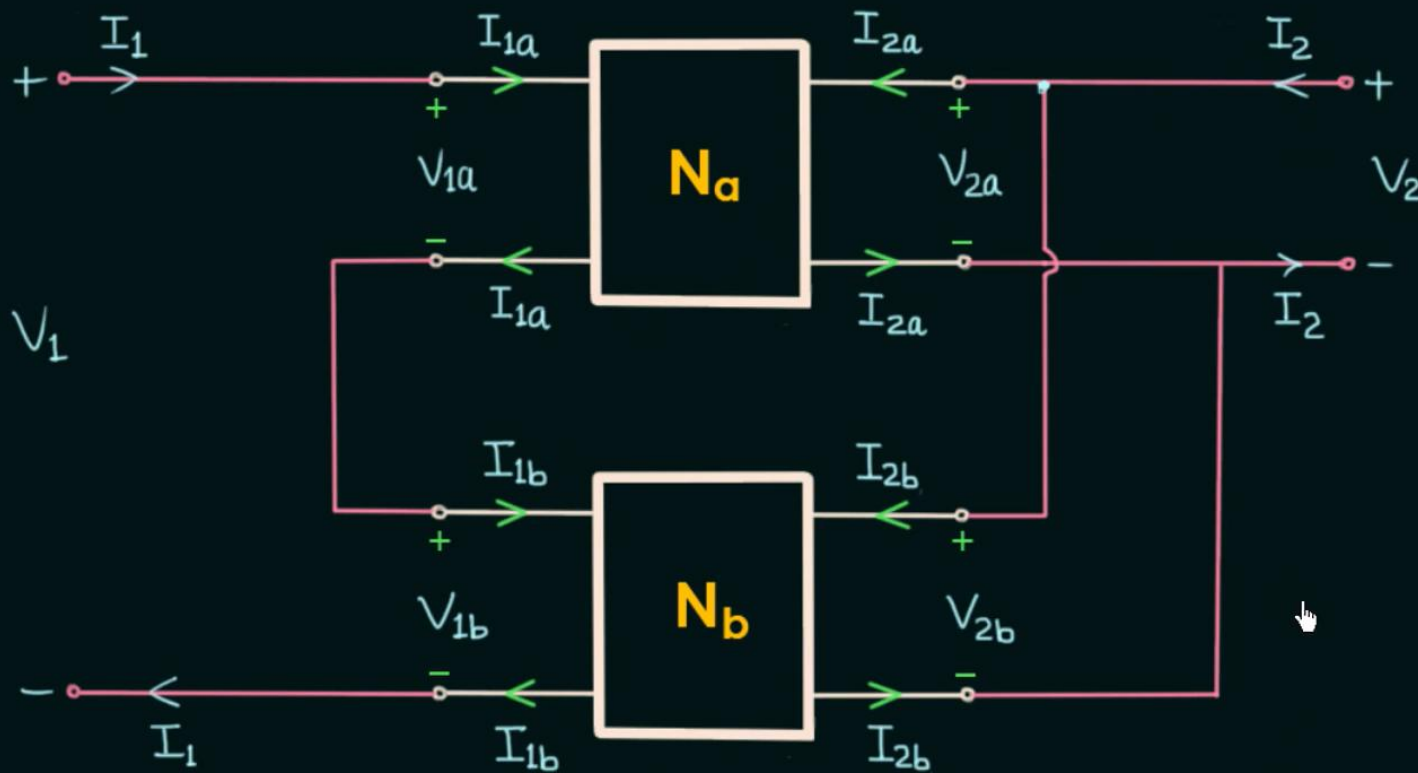

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{2a} \end{bmatrix} + \begin{bmatrix} V_{1b} \\ I_{2b} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [H_a] \begin{bmatrix} I_{1a} \\ V_{2a} \end{bmatrix} + [H_b] \begin{bmatrix} I_{1b} \\ V_{2b} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \underbrace{\{[H_a] + [H_b]\}}_{[H]} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$[H] = [H_a] + [H_b]$$

$$[H] = [H_a] + [H_b] + \dots + [H_n]$$

$$I_1 = I_{1a} = I_{1b}$$


$$V_1 = V_{1a} + V_{1b} \quad \text{--- (I)}$$

$$V_2 = V_{2a} = V_{2b}$$

$$I_2 = I_{2a} + I_{2b} \quad \text{--- (II)}$$

## Parallel-Series Interconnection

To exit full screen, press Esc

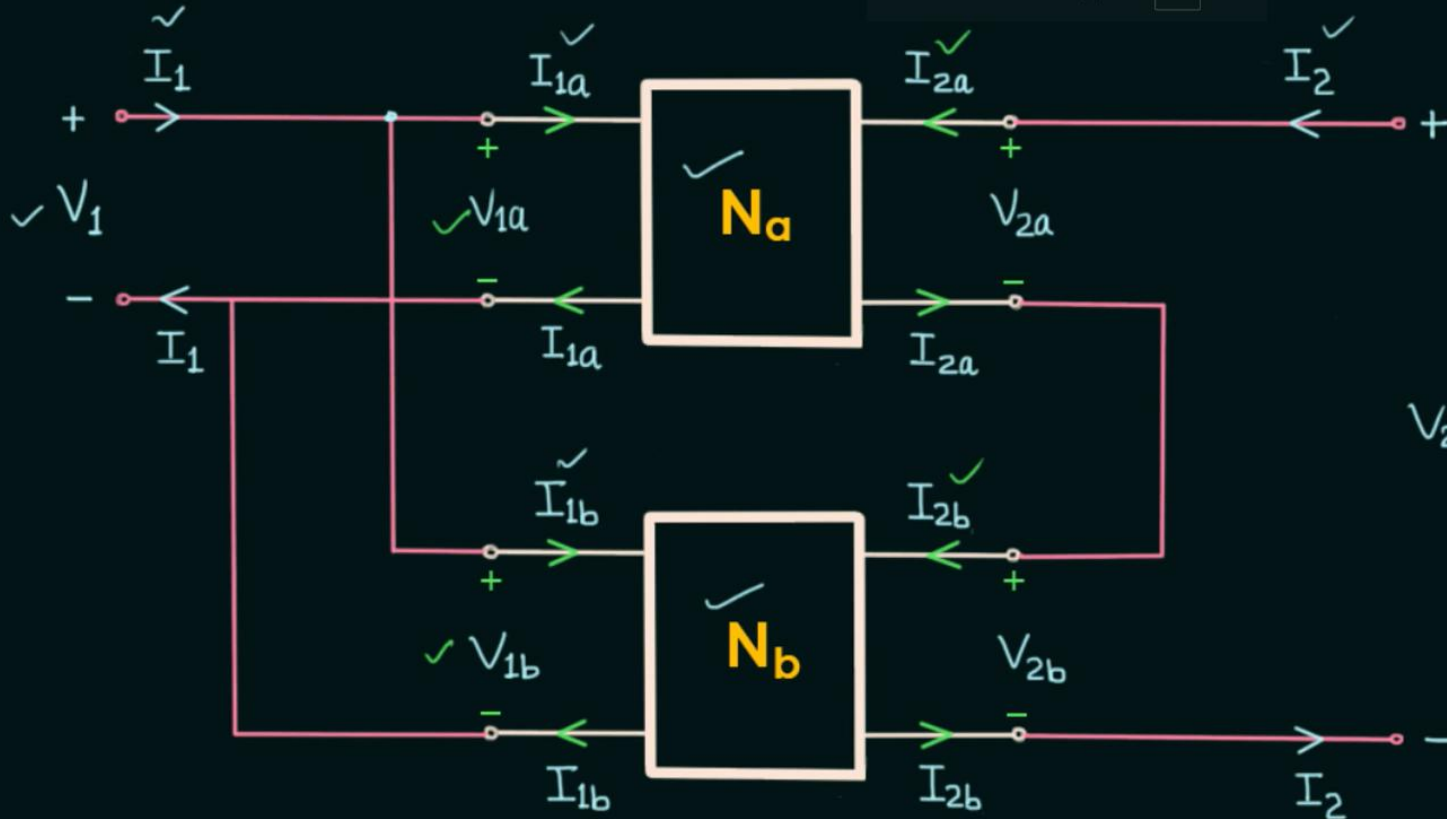

$$V_1 = V_{1a} = V_{1b}$$

$$I_2 = I_{2a} = I_{2b}$$

$$I_1 = I_{1a} + I_{1b} \quad \text{--- (i)}$$

$$V_2 = V_{2a} + V_{2b} \quad \text{--- (ii)}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} I_{1b} \\ V_{2b} \end{bmatrix}$$

$$[G_a] \begin{bmatrix} V_{1a} \\ I_{2a} \end{bmatrix} + [G_b] \begin{bmatrix} V_{1b} \\ I_{2b} \end{bmatrix}$$

$V_2$  ✓


$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [G_a] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} + [G_b] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \underbrace{\{ [G_a] + [G_b] \}}_{[G]} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$[G] = [G_a] + [G_b]$$

$$[G] = [G_a] + [G_b] + \dots + [G_n]$$

## ✓ Cascade Interconnection

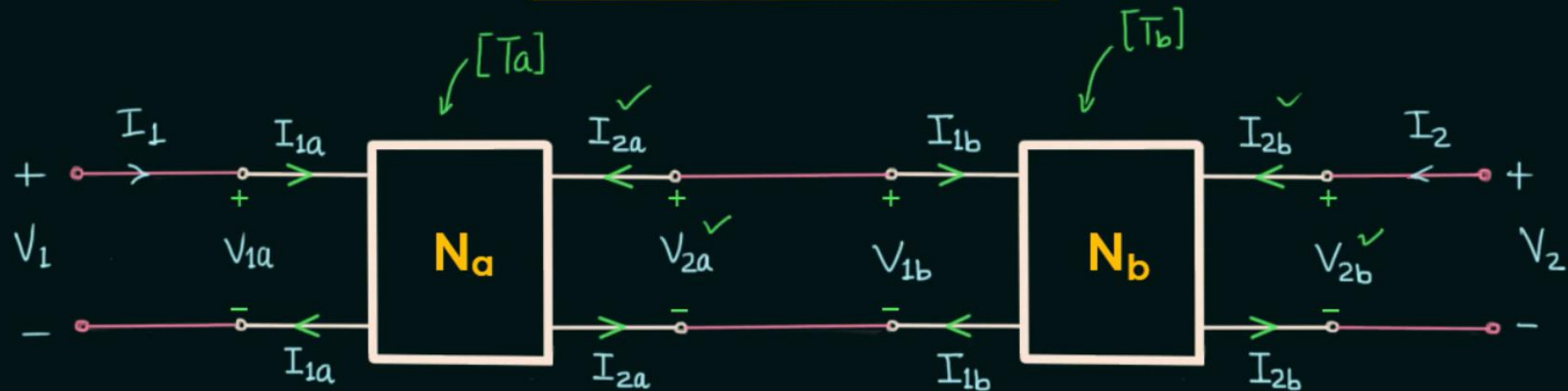

$$V_1 = V_{1a}, \quad I_1 = I_{1a}, \quad V_{2a} = V_{1b}, \quad I_{2a} = -I_{1b}, \quad V_{2b} = V_2 \quad \text{and} \quad I_{2b} = I_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [T_a] \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$\swarrow V_{1b}$   
 $\nwarrow I_{1b}$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [T_a] \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [T_a] [T_b] \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$\swarrow V_2$   
 $\nwarrow -I_2$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \underbrace{[T_a] \times [T_b]}_{[T]} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

*imp.*

$$[T] = [T_a] \times [T_b]$$



# ✓ Bartlett's Bisection Theorem

Z-par.

>> Albert Charles Bartlett


lattice n/w ?

Shunt el. ?

>> Applicable to symmetrical two-port networks


>> Basic symmetrical lattice

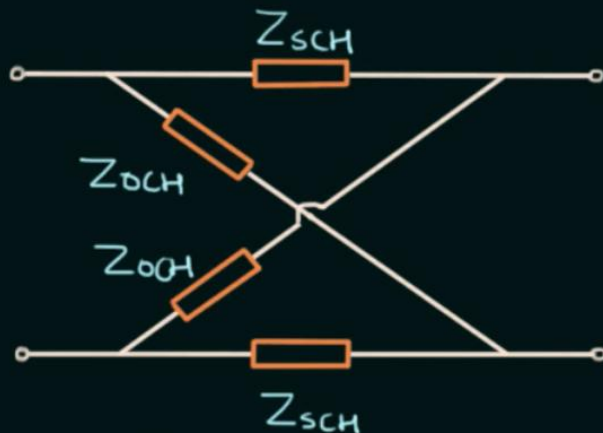✓ Step 3: Construct basic symmetrical lattice using  $Z_{OCH}$  &  $Z_{SCH}$ .





$$Z_{11} = Z_{22} = \frac{Z_{OCH} + Z_{SCH}}{2} \quad Z_{12} = Z_{21} = \frac{Z_{OCH} - Z_{SCH}}{2}$$

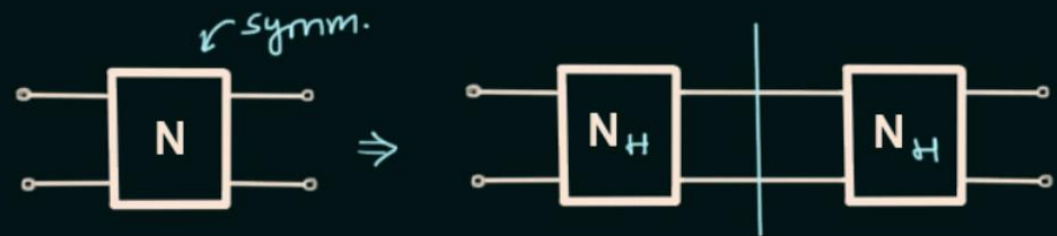✓ Step 1: Separate the n/w into two equal parts.



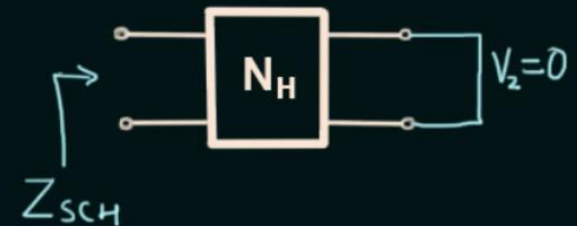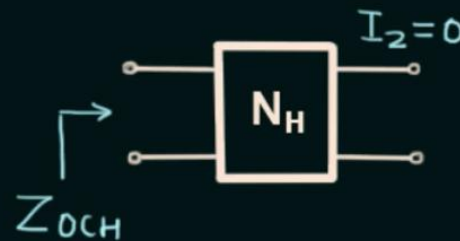
✓ Step 2: Bisect and find out  $Z_{OCH}$  &  $Z_{SCH}$ .


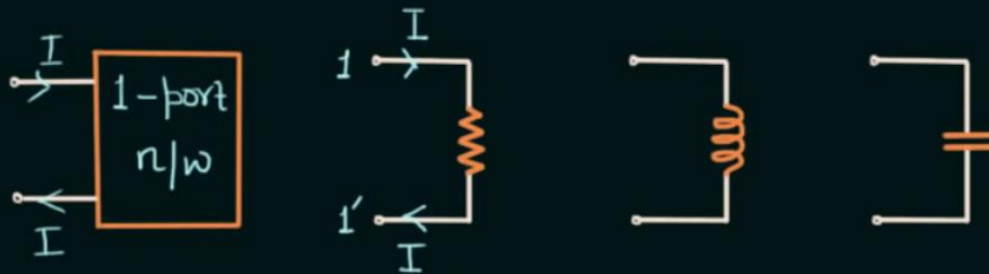
## Introduction to Two-Port Networks

**Port:** <sup>2 ↗</sup> Pair of terminals through which a current may enter or leave the network.

**1-Port N/W:** Two terminal devices such as R, L and C forms 1-port network.




$$\text{net current} = I + (-I) = 0A$$

➤ Current entering from one terminal must leave from the other terminal.

the black box may also contain the dependent sources but never contain an

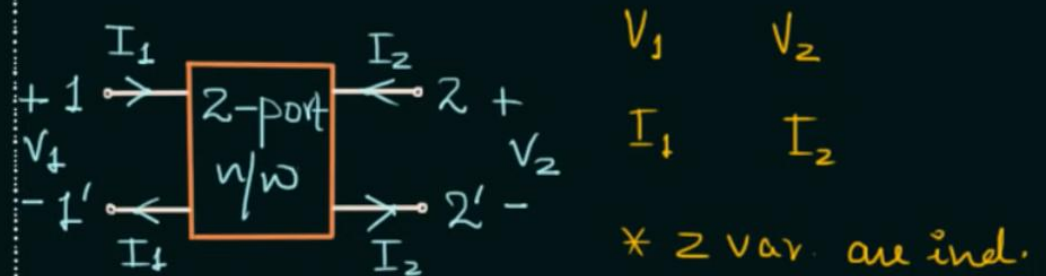**2-Port N/W:** Two-port networks have two separate ports.



➤ Black box should consist only linear (bidirectional) and passive elements.

➤ Black box may contain energy storing elements. L and C


➤ Black box may also contain dependent sources, but never contain an independent source.

## Z Parameters (or) Impedance Parameters (or) Open ckt. parameters

$I_1^\vee$  and  $I_2^\vee \rightarrow \text{ind.}$

$V_1$  and  $V_2 \rightarrow \text{dep.}$
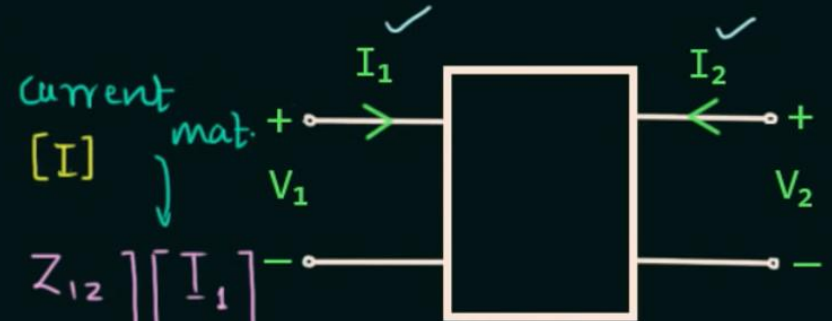
$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \mathbf{Z} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$



$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (2)}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow [V] = [Z][I]$$

$\uparrow$  voltage mat.  $\uparrow$  impedance matrix  
[V] [Z]

$$V_1 - Z_{11}I_1 - Z_{12}I_2 = 0$$

$$V_2 - Z_{21}I_1 - Z_{22}I_2 = 0$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

Open circuit driving pt. i/p imp.

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$


Open circuit forward tr. imp.

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

Open circuit rev. tr. imp.

(H.W.)

$$Z_{22} = ?$$

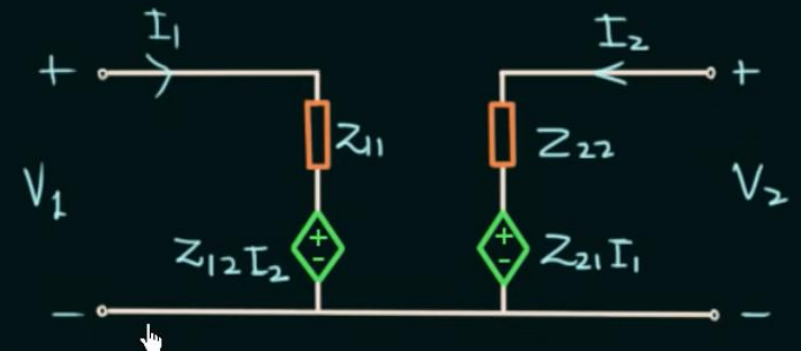

## ✓ Z-Parameters (Solved Problem 1)

**Question:** Find the Z-parameters of the below given two-port network.



$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$$[Z] = \begin{bmatrix} 6 & 4 \\ 4 & 10 \end{bmatrix} \text{ ans.}$$

**Solution:**  $+V_1 - 2I_1 - 4(I_1 + I_2) = 0$

$$V_1 = \underline{6}I_1 + \underline{4}I_2 \text{ — (1)}$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$+V_2 - 6I_2 - 4(I_1 + I_2) = 0$$

$$V_2 = \underline{4}I_1 + \underline{10}I_2 \text{ — (2)}$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$





## ✓ Z-Parameters (Solved Problem 2)

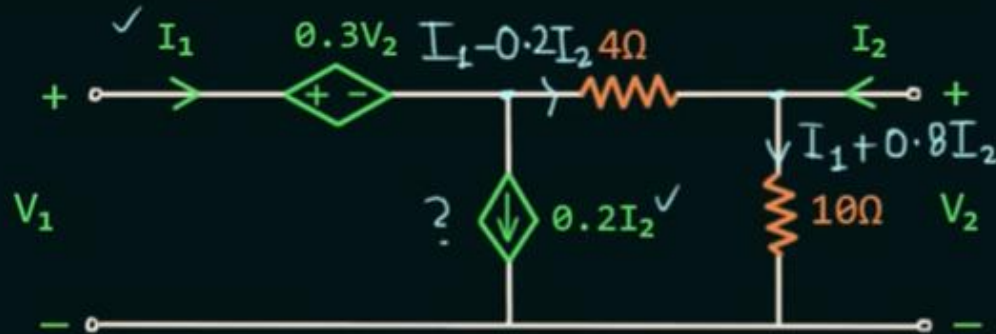**Question:** The Z-parameter matrix of the two-port network as shown below is



$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

**Solution:**

$$+V_1 - 0.3V_2 - 4(I_1 - 0.2I_2) - 10(I_1 + 0.8I_2) = 0$$

$$V_1 - 0.3V_2 - 14I_1 - 7.2I_2 = 0 \quad \text{--- (1)}$$

$$V_1 - 0.3(10I_1 + 8I_2) - 14I_1 - 7.2I_2 = 0$$

$$V_1 = 17I_1 + 9.6I_2 \quad \text{--- (3)}$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$+V_2 - 10(I_1 + 0.8I_2) = 0$$

$$V_2 = 10I_1 + 8I_2 \quad \text{--- (2)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$[Z] = \begin{bmatrix} 17 & 9.6 \\ 10 & 8 \end{bmatrix}$$


## Y-Parameters (or) Admittance Parameters

$V_1$  and  $V_2 \rightarrow$  ind.

$I_1$  and  $I_2 \rightarrow$  dep.

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = f \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$[I] = [Y][V]$$

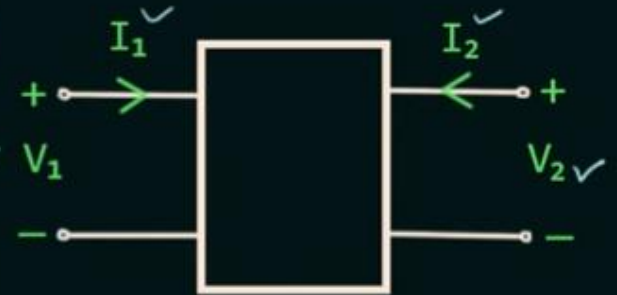

curr. curr. curr.

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$\nwarrow$  admittance matrix

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

Short ckt. Driving pt. i/p ad.

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$


Short ckt. for. tr. ad.

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

Short ckt. rev. tr. ad.

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

Short ckt. driving pt. o/p ad.

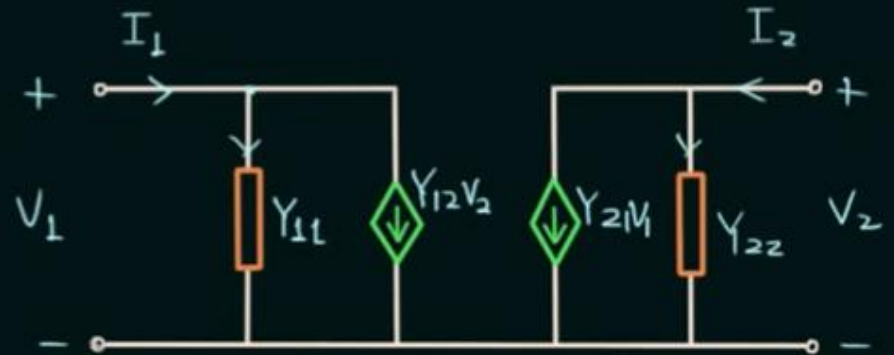

## ✓ Y-Parameters to Z-Parameters Conversion

$$✓ [V] = [Z][I] \quad \text{and} \quad [I] = [Y][V] \Rightarrow ✓ [V] = [Y]^{-1}[I]$$

$$\text{imp.} \quad ✓ [Z] = [Y]^{-1}$$

$$\begin{aligned} \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} &= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1} \\ &= \frac{\text{adj}(Y)}{|Y|} \\ &= \frac{1}{|Y|} \begin{bmatrix} (-1)^{1+1} Y_{22} & -Y_{21} \\ -Y_{12} & Y_{11} \end{bmatrix}^T_{2 \times 2} \end{aligned}$$

$$\begin{aligned} \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} &= \frac{1}{|Y|} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix} \\ &\quad \downarrow \\ &\quad Y_{11} \times Y_{22} - Y_{21} \times Y_{12} \\ Z_{11} &= \frac{Y_{22}}{|Y|} & Z_{21} &= -\frac{Y_{21}}{|Y|} \\ Z_{12} &= -\frac{Y_{12}}{|Y|} & Z_{22} &= \frac{Y_{11}}{|Y|} \end{aligned}$$

## ✓ Z-Parameters to Y-Parameters Conversion

$$✓ [V] = [Z][I] \quad \text{and} \quad ✓ [I] = [Y][V]$$

↓

$$✓ [I] = [Z]^{-1} [V] \quad \text{imp. } [Y] = [Z]^{-1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}_{2 \times 2} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}_{2 \times 2}^{-1}$$

$\text{adj}(A)/|A|$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \frac{1}{|Z|} \begin{bmatrix} Z_{22} & -Z_{21} \\ -Z_{12} & Z_{11} \end{bmatrix}^T$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \frac{1}{|Z|} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$$

$$Y_{11} = \frac{Z_{22}}{|Z|}$$

$$Y_{21} = -\frac{Z_{21}}{|Z|}$$

$$Y_{12} = -\frac{Z_{12}}{|Z|}$$

$$Y_{22} = \frac{Z_{11}}{|Z|}$$



## ✓ h-Parameters (or) Hybrid Parameters

$I_1$  and  $V_2$  → ind.

$V_1$  and  $I_2$  → dep.

$$\begin{pmatrix} V_1 \\ I_2 \end{pmatrix} = f \begin{pmatrix} I_1 \\ V_2 \end{pmatrix}$$

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \quad \text{--- KVL eqn} \quad \text{--- (I)} \\ I_2 &= h_{21} I_1 + h_{22} V_2 \quad \text{--- KCL eqn} \quad \text{--- (II)} \end{aligned} \Rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$




$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{Short ckt. driving pt. i/p imp.}$$

$$* h_{11} = \frac{1}{I_1/V_1|_{V_2=0}} \Rightarrow h_{11} = 1/Y_{11}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \text{Short ckt. for current gain.}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \text{Open ckt. rev. voltage gain.}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad \text{(H.W.)} \quad * h_{22} = \frac{1}{V_2/I_2|_{I_1=0}} \Rightarrow h_{22} = 1/Z_{22}$$

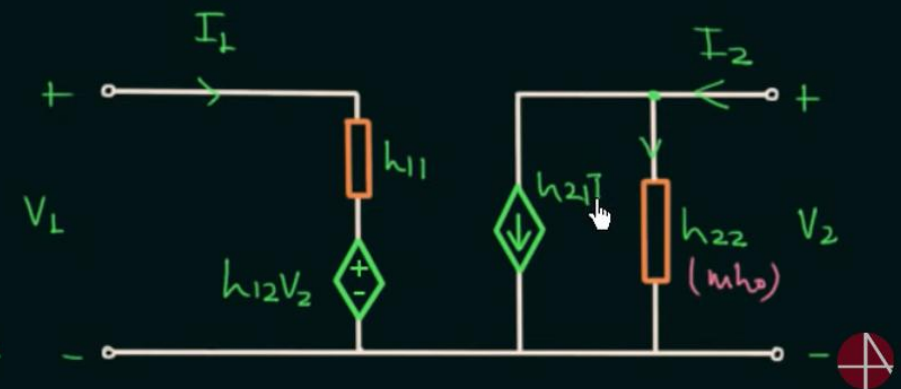

## h-Parameters to Z-Parameters Conversion

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- ①}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- ②}$$

rearrange eq<sup>n</sup> ② -

$$-h_{21} I_1 + I_2 = h_{22} V_2$$

$$V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \quad \text{--- ③} \checkmark$$

$$V_2 \rightarrow \text{①}$$

$$V_1 = h_{11} I_1 + h_{12} \left[ -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right]$$

$$V_1 = h_{11} I_1 - \frac{h_{21} h_{12}}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- ④} \checkmark$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- ⑤} \checkmark$$

$$V_1 = \left[ h_{11} - \frac{h_{21} h_{12}}{h_{22}} \right] I_1 + \frac{h_{12}}{h_{22}} I_2$$

$\frac{h_{11} h_{22} - h_{21} h_{12}}{h_{22}} = \frac{|H|}{h_{22}}$

$$V_1 = \frac{|H|}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2 \quad \text{--- ⑥} \checkmark$$

$$Z_{11} = \frac{|H|}{h_{22}}$$

$$Z_{12} = \frac{h_{12}}{h_{22}}$$

$Z \rightarrow h$

$$h_{11} = \frac{|Z|}{Z_{22}}$$

$$h_{12} = \frac{Z_{12}}{Z_{22}}$$

$$h_{21} = -Z_{21}/Z_{22}$$

$$h_{22} = 1/Z_{22}$$

$$Z_{21} = -\frac{h_{21}}{h_{22}}$$

$$Z_{22} = \frac{1}{h_{22}}$$

## h-Parameters to Y-Parameters Conversion

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (i)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (ii)}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (iii)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (iv)}$$

$$V_1 - h_{12} V_2 = h_{11} I_1$$

$$\Rightarrow I_1 = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \quad \text{--- (v)}$$

$$I_1 \rightarrow \text{--- (v) ---}$$

$$I_2 = h_{21} \left[ \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \right] + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 - \frac{h_{21} h_{12}}{h_{11}} V_2 + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 + \left[ h_{22} - \frac{h_{21} h_{12}}{h_{11}} \right] V_2$$

$\frac{h_{11} h_{22} - h_{21} h_{12}}{h_{11}} = \frac{|H|}{h_{11}}$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 + \frac{|H|}{h_{11}} V_2 \quad \text{--- (vi)}$$

$$Y_{11} = \frac{1}{h_{11}} \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

$$Y_{21} = \frac{h_{21}}{h_{11}} \quad Y_{22} = \frac{|H|}{h_{11}}$$

$Y \rightarrow h$

$$h_{11} = 1/Y_{11}$$

$$h_{12} = -Y_{12}/Y_{11}$$

$$h_{21} = Y_{21}/Y_{11}$$

$$h_{22} = |Y|/Y_{11}$$

## ✓ g-Parameters (or) Inverse Hybrid Parameters

$V_1$  and  $I_2 \rightarrow \text{ind.}$

$I_1$  and  $V_2 \rightarrow \text{dep.}$

$$\begin{pmatrix} I_1 \\ V_2 \end{pmatrix} = f \begin{pmatrix} V_1 \\ I_2 \end{pmatrix}$$

$$I_1 = g_{11} V_1 + g_{12} I_2 \quad \text{--- KCL ---} \quad \textcircled{I}$$

$$V_2 = g_{21} V_1 + g_{22} I_2 \quad \text{--- KVL ---} \quad \textcircled{II}$$

$$\Rightarrow \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$



$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \quad \text{Open ckt. dr. pt. i/p ad.}$$

$$g_{11} = \frac{1}{V_1/I_1|_{I_2=0}} \Rightarrow g_{11} = \frac{1}{Z_{11}}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad \text{Open ckt. for. vol. gain}$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} \quad \text{Short Ckt. rev. cur. gain}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} \quad \text{Short ckt. dr. pt. o/p imp.}$$

$$* g_{22} = \frac{1}{I_2/V_2|_{V_1=0}} \Rightarrow g_{22} = 1/Y_{22}$$

